

Technology



Dr. Denise Meeks

tucsonkosmicgirl@gmail.com

http://denisemeeks.com/science/notebooks/notebook_technology.pdf

Technology: Base 2 and Base 10

IEC prefix		representations				customary prefix	
name	symbol	base 2	base 1024	value	base 10	name	symbol
kibi	Ki	2 ¹⁰	1024 ¹	1024	≈ 1.02×10 ³	kilo	k or K
mebi	Mi	2 ²⁰	1024 ²	1048576	≈ 1.05×10 ⁶	mega	M
gibi	Gi	2 ³⁰	1024 ³	1073741824	≈ 1.07×10 ⁹	giga	G
tebi	Ti	2 ⁴⁰	1024 ⁴	1099511627776	≈ 1.10×10 ¹²	tera	T
pebi	Pi	2 ⁵⁰	1024 ⁵	1125899906842624	≈ 1.13×10 ¹⁵	peta	P
exbi	Ei	2 ⁶⁰	1024 ⁶	1152921504606846976	≈ 1.15×10 ¹⁸	exa	E
zebi	Zi	2 ⁷⁰	1024 ⁷	1180591620717411303424	≈ 1.18×10 ²¹	zetta	Z
yobi	Yi	2 ⁸⁰	1024 ⁸	1208925819614629174706176	≈ 1.21×10 ²⁴	yotta	Y

Technology: Electric Force and Charge

q ₁ /q ₂ charges	force on q ₁ charge	force on q ₂ charge	result
- / -	← ⊖	⊖ →	repulsion
+ / +	← ⊕	⊕ →	repulsion
- / +	⊖ →	← ⊕	attraction
+ / -	⊕ →	← ⊖	attraction

particle	charge (C)	charge (e)
Electron	1.602×10 ⁻¹⁹ C	-e
Proton	1.602×10 ⁻¹⁹ C	+e
Neutron	0 C	0

Technology: Coulomb's Law

$$\text{Coulomb's law } F = \frac{kq_1q_2}{r^2}$$

F = force in newtons (N)

$$k = 8.988 \times 10^9 \text{ N} \cdot \text{m}^2 / \text{C}^2$$

q_1 = first charge in coulombs (C).

q_2 = second charge in coulombs (C).

r = distance between the 2 charges in meters (m)

$$1 \text{ C} = 6.242 \times 10^{18} \text{ electrons}$$

Technology: Ohm's Law, Power, and DC Circuits

Direct current (DC) is used to power electronics and other digital equipment, smartphones, tablets, electric vehicles, LED and LCD TVs, and is generated by a constant voltage source like a battery or other DC voltage source.

$$V_R = I_R \times R$$

$$\text{power } P = IV = I^2 R$$

V_R = voltage drop in volts (V)

I_R = current in amps (A)

R = resistance in ohms (Ω)

Technology: Voltage and Current in DC Circuits

voltage in series $V_S = V_1 + V_2 + V_3 + \dots$

voltage in parallel $V_P = V_1 = V_2 = V_3 = \dots$

voltage divider for loads in series $V_i = V_{total} \frac{R_i}{R_{total}}$

current in series $I_S = I_1 = I_2 = I_3 = \dots$

current in parallel $I_P = I_1 + I_2 + I_3 + \dots$

current divider of resistors in parallel $I_i = I_P \frac{R_P}{R_i + R_P}$

Technology: Resistance and Capacitance in DC Circuits

resistance in series $R_{total} = R_1 + R_2 + R_3 + \dots$

resistance in parallel $R_{total} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3 + \dots}$

capacitance in parallel $C_P = C_1 + C_2 + C_3 + \dots$

capacitance in series $C_S = \frac{1}{1/C_1 + 1/C_2 + 1/C_3 + \dots}$

inductance in parallel $L_P = \frac{1}{1/L_1 + 1/L_2 + 1/L_3 + \dots}$

inductance in series $L_S = L_1 + L_2 + L_3 + \dots$

Technology: Capacitance in DC Circuits

charge on a capacitor $q_{flow}(t) = Q_{max}(1 - e^{-t/RC})$

$$Q_{max} = CV_0 \quad C = \frac{Q}{V_c}$$

capacitors in series $\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$

capacitors in parallel $C_{total} = C_1 + C_2 + C_3 + \dots$

Technology: Wheatstone Bridge

$$R_x = \frac{R_2}{R_1} \times R_3$$


$$I_3 - I_x + I_G = 0 \quad I_1 - I_2 - I_G = 0$$

$$I_3 R_3 - I_G R_G - I_1 R_1 = 0$$

$$I_x R_x - I_2 R_2 + I_G R_G = 0$$

when bridge balanced $I_G = 0 \quad I_3 R_3 = I_1 R_1 \quad I_x R_x = I_2 R_2$
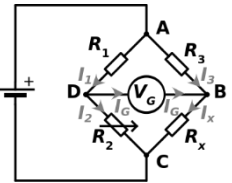
$$V_G = \left(\frac{R_2}{R_1 + R_2} - \frac{R_x}{R_x + R_3} \right) V_S$$



(Image source:

https://en.wikipedia.org/wiki/Wheatstone_bridge#/media/File:Wheatstonebridge_curr_ent.svg, Rhdv and cmglee, CC BY SA 3.0)

Technology: RC Transient Response in DC Circuits with Switches

series, RC charging	series, RC discharging
$\tau = RC$	$\tau = RC$
$e^{-N} = e^{-t/\tau} = e^{-t/RC}$	$e^{-N} = e^{-t/\tau} = e^{-t/RC}$
$V_{bat} = V_R(t) + V_C(t)$	$0 = V_R(t) + V_C(t)$
$I(t) = \frac{V_{bat} - V_0}{R} e^{-N}$	$I(t) = \frac{V_0}{R} e^{-N}$
$V_R(t) = I(t)R = (V_{bat} - V_0)e^{-N}$	$V_R(t) = -V_0 e^{-N}$
$V_C(t) = V_0 + (V_{bat} - V_0)(1 - e^{-N})$	$V_C(t) = V_0 e^{-N}$
$Q_C(t) = C[V_0 + (V_{bat} - V_0)(1 - e^{-N})]$	$Q_C(t) = CV_0 e^{-N}$

Technology: RL Transient Response in DC Circuits with Switches

series, RL charging	series, RL discharging
$\tau = L/R$	$\tau = L/R$
$e^{-N} = e^{-t/\tau} = e^{-tR/L}$	$e^{-N} = e^{-t/\tau} = e^{-tR/L}$
$V_{bat} = V_R(t) + V_L(t)$	$0 = V_R(t) + V_L(t)$
$I(t) = I_0 e^{-N} + \frac{V_{bat}}{R}(1 - e^{-N})$	$I(t) = I_0 e^{-N}$
$V_R(t) = I(t)R = I_0 R e^{-N} + V_{bat}(1 - e^{-N})$	$V_R(t) = I_0 R e^{-N}$
$V_L(t) = (V_{bat} - I_0 R)e^{-N}$	$V_L(t) = -I_0 R e^{-N}$

Technology: Voltage in AC Circuits

voltage $V(t) = V_{max} \sin(\omega t) = \frac{I_{max}}{\omega C} \sin(\omega t) = \frac{I_{max}}{2\pi f} \sin(\omega t)$

$V(t)$ = voltage at time t (volts)

V_{max} = maximal voltage (amplitude of sine)

ω = angular frequency in radians per second (rad/s)

t = time in seconds (s)

f = frequency in Hz

$$V_{RMS} = V_{max} / \sqrt{2} = 0.707 V_{max}$$

peak-to-peak voltage $V_{P-P} = V_{max}$

average power $P_{avg} = I_{RMS}^2 R$

Technology: Capacitors in AC Circuits

$$I_{RMS} = \frac{V_{RMS}}{X_C}$$

capacitive reactance $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

f = frequency in Hz

ω = angular frequency in radians per second (rad/s)

C = capacitance in farads (F)

Technology: RC Circuits

capacitance reactance $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$ in ohms (Ω)

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} = \frac{V_{RMS}}{I_{RMS}}$$

phase angle $\cos \phi = \frac{R}{Z}$ $Z =$ impedance in ohms (Ω)

$R =$ resistance in ohms (Ω) $C =$ capacitance in farads (F)

$$V_{max} = I_{max} \sqrt{R^2 + X_C^2} = I_{max} Z$$

$$V_{RMS} = I_{RMS} \sqrt{R^2 + X_C^2} = \sqrt{V_{RMS,R}^2 + V_{RMS,C}^2} = I_{RMS} Z$$

$$\text{average power } P_{avg} = I_{RMS} V_{RMS} \cos \phi$$

Technology: Inductors in AC Circuits

inductive reactance $X_L = \omega L = 2\pi f L$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + (\omega L)^2} = \frac{V_{RMS}}{I_{RMS}}$$

phase angle $\cos \phi = \frac{R}{Z}$ $Z =$ impedance in ohms (Ω)

$R =$ resistance in ohms (Ω) $L =$ inductance in henrys (H)

$$V_{max} = I_{max} \sqrt{R^2 + X_L^2} = I_{max} Z$$

$$V_{RMS} = I_{RMS} \sqrt{R^2 + X_L^2} = \sqrt{V_{RMS,R}^2 + V_{RMS,L}^2} = I_{RMS} Z$$

Technology: Current in AC Circuits

instantaneous current $I(t) = I_{max} \sin(\omega t)$

$I(t) =$ current at time t in amps (A).

$I_{max} =$ maximal current (amplitude of sine)

$\omega =$ angular frequency in radians per second (rad/s)

$t =$ time in seconds (s)

$$\text{RMS current } I_{RMS} = \frac{V_{RMS}}{X_C} = V_{RMS} \omega C$$

peak-to-peak current $I_{p-p} = I_{peak}$

Technology: RLC Circuits and Resonance

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_0$$

$f_0 =$ resonant frequency, frequency at which $X_L = X_C$

Technology: Resistivity

$$R = \frac{\rho L}{A}$$

for metallic conductors, the resistivity and resistance vary linearly with changes in temperature

$$\rho = \rho_0 [1 + \alpha(T - T_0)]$$

$$R = R_0 [1 + \alpha(T - T_0)]$$

$\rho_0 =$ resistivity at T_0

$R_0 =$ resistance at T_0

$\alpha =$ temperature coefficient

Technology: Boolean Algebra (1)

x	y	$\neg x$	$\neg y$	$x \wedge y$	$\neg x \wedge y$	$x \wedge \neg y$	$x \vee y$	$\neg x \vee y$	$x \vee \neg y$
0	0	1	1	0	0	0	0	1	1
1	0	0	1	0	0	1	1	0	1
0	1	1	0	0	1	0	1	1	0
1	1	0	0	1	0	0	1	1	1

x	y	$x \rightarrow y$	$x \oplus y$	$\neg x \oplus \neg y$	$x \equiv y$	$\neg x \equiv \neg y$
0	0	1	0	0	1	0
1	0	0	1	1	0	1
0	1	1	1	1	0	1
1	1	1	0	0	1	0

Technology: Boolean Algebra (2)

$x \wedge y =$ x AND y $x \vee y =$ x OR y $x \oplus y =$ x EXCLUSIVE OR y

$\neg x =$ NOT x $x \equiv y =$ x EQUALS y

$x \wedge y = \neg(\neg x \vee \neg y) = xy = \min(x, y)$

$x \vee y = \neg(\neg x \wedge \neg y) = x + y - xy = \max(x, y)$

$x \rightarrow y = \neg x \vee y$

$\neg x = 1 - x$

$x \oplus y = (x \vee y) \wedge \neg(x \wedge y)$

$x \equiv y = \neg(x \oplus y)$

Demorgan's laws:

$\neg(x \wedge y) = \neg x \vee \neg y$

$\neg(x \vee y) = \neg x \wedge \neg y$